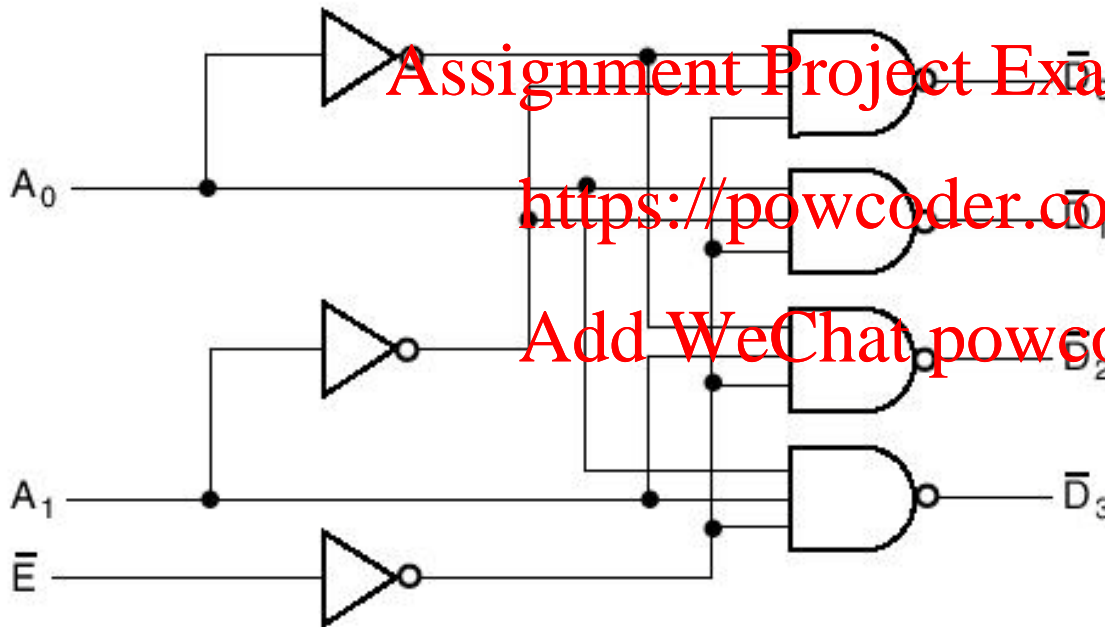


# 2 to 4 Line Decoder Structural



$\bar{E}$	$A_1$	$A_0$	$\bar{D}_0$	$\bar{D}_1$	$\bar{D}_2$	$\bar{D}_3$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{\bar{E} \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{\bar{E} \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{\bar{E} A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{\bar{E} A_1 A_0}$$

# 2 to 4 Line Decoder (Page 1)

## Structural

-- 2-to-4 Line Decoder: Structural VHDL Description

library ieee, lcdf\_vhdl;

use ieee.std\_logic\_1164.all; lcdf\_vhdl.pkg\_prims.all;

entity decoder\_2\_to\_4 is

port(E, A0, A1: in std\_logic;  
D0, D1, D2, D3: out std\_logic);

end decoder\_2\_to\_4;

architecture structural\_1 of decoder\_2\_to\_4 is

component NOT1

port(in1: in std\_logic;  
out1: out std\_logic);

end component;


# 2 to 4 Line Decoder (Page 3)

## Structural

```
component NAND3
  port(in1, in2, in3: in std_logic;
        out1: out std_logic);
end component;

signal not_A0, not_A1: std_logic;
begin
  g0: NOT1 port map (in1 => A0, out1 => not_A0);
  g1: NOT1 port map (in1 => A1, out1 => not_A1);
  g2: NAND3 port map (in1 => not_A0, in2 => not_A1,
                     in3 => E, out1 => D0);
  g3: NAND3 port map (in1 => A0, in2 => not_A1,
                     in3 => E, out1 => D1);
  g4: NAND3 port map (in1 => not_A0, in2 => A1,
                     in3 => E, out1 => D2);
  g5: NAND3 port map (in1 => A0, in2 => A1,
                     in3 => E, out1 => D3);
end structural_1;
```

# 4 to 1 Line Multiplexer

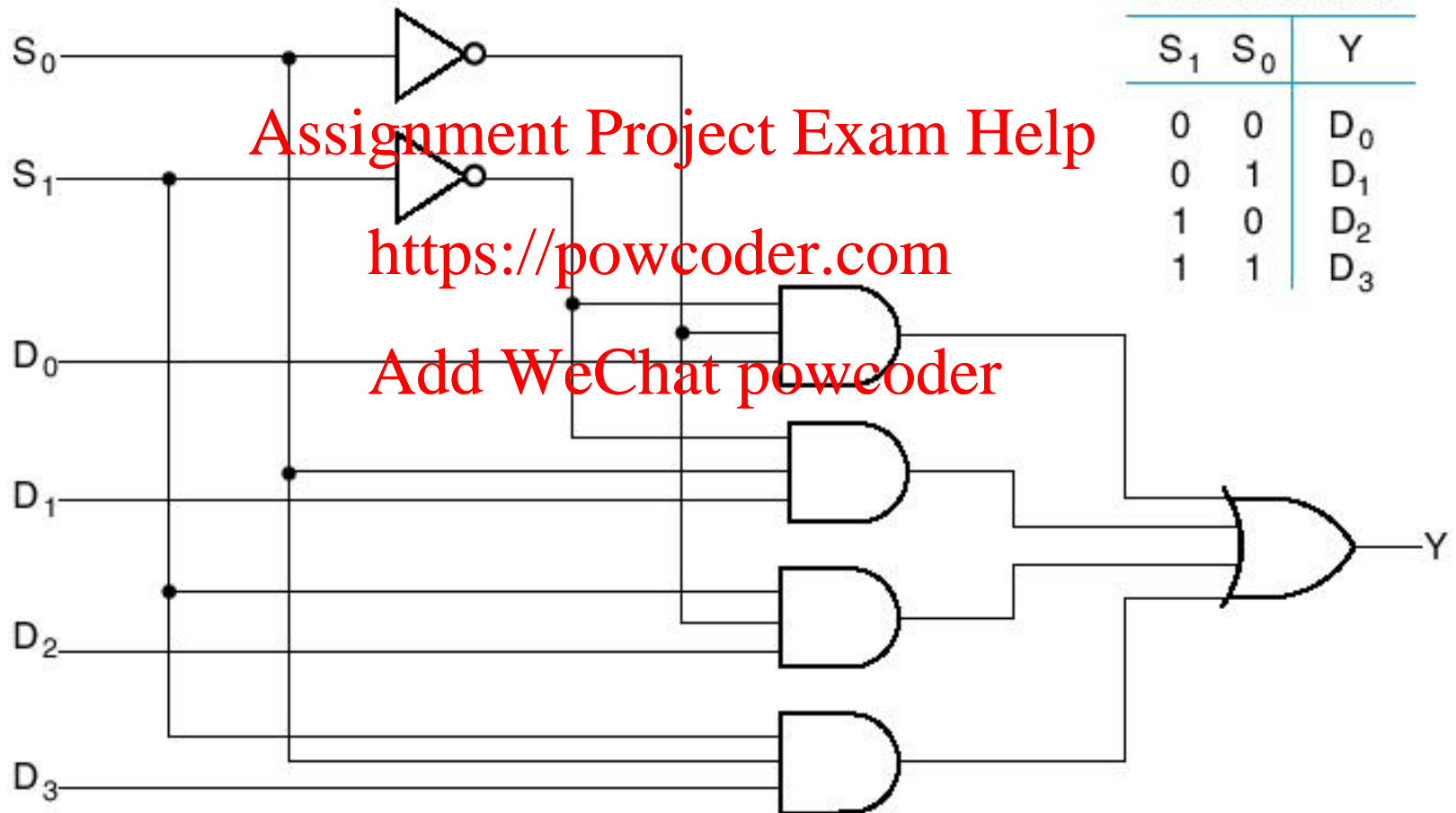

Function table

$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

# 4 to 1 Line Multiplexer (Page 1)

## -- 4-to-1 Line Multiplexer: Structural VHDL Description

```
library ieee, lcdf_vhdl;
```

```
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;
```

```
entity multiplexer_4_to_1 is
```

```
    port(S: in std_logic_vector(0 to 1);
```

```
          D: in std_logic_vector(0 to 3);
```

```
          Y: out std_logic);
```

```
end multiplexer_4_to_1_st;
```

```
architecture structural_2 of multiplexer_4_to_1_st is
    component NOT1
```

```
        port(in1: in std_logic;
```

```
              out1: out std_logic);
```

```
    end component;
```

```
    component AND3
```

```
        port(in1, in2, in3: in std_logic;
```

```
              out1: out std_logic);
```

```
    end component;
```

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# 4 to 1 Line Multiplexer (Page 2)


```
component OR4
port(in1, in2, in3, in4: in std_logic;
out1: out std_logic);
end component;
```

```
signal not_S: std_logic_vector(0 to 1);
signal N: std_logic_vector(0 to 3);
begin
g0: NOT1 port map (S(0), not_S(0));
g1: NOT1 port map (S(1), not_S(1));
g2: AND3 port map (not_S(1), not_S(0), D(0), N(0));
g3: AND3 port map (not_S(1), S(0), D(1), N(1));
g4: AND3 port map (S(1), not_S(0), D(2), N(2));
g5: AND3 port map (S(1), S(0), D(3), N(3));
g6: OR4 port map (N(0), N(1), N(2), N(3), Y);
end structural_2;
```

# 2 to 4 Line Decoder

## Dataflow

Same as slide 1

 

$\bar{E}$	$A_1$	$A_0$	$\bar{D}_0$	$\bar{D}_1$	$\bar{D}_2$	$\bar{D}_3$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{\bar{E} \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{\bar{E} \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{\bar{E} A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{\bar{E} A_1 A_0}$$



# 2 to 4 Line Decoder(Page 1)

## Dataflow

-- 2-to-4 Line Decoder: Dataflow VHDL Description

library ieee, lcdf\_vhdl;

use ieee.std\_logic\_1164.all, lcdf\_vhdl.func\_prims.all;

entity decoder\_2\_to\_4 is

port(E, A0, A1: in std\_logic;  
D0, D1, D2, D3: out std\_logic);

end decoder\_2\_to\_4;

architecture dataflow\_1 of decoder\_2\_to\_4 is

signal not\_A0, not\_A1: std\_logic;

begin

not\_A0 <= not A0;

not\_A1 <= not A1;

D0 <= not (not\_A0 and not\_A1 and E);

D1 <= not (A0 and not\_A1 and E);

D2 <= not (not\_A0 and A1 and E);

D3 <= not (A0 and A1 and E);


end dataflow\_1;



# 4 to 1 Line Multiplexer

## Conditional Dataflow (When-Else)

Same as slide 4

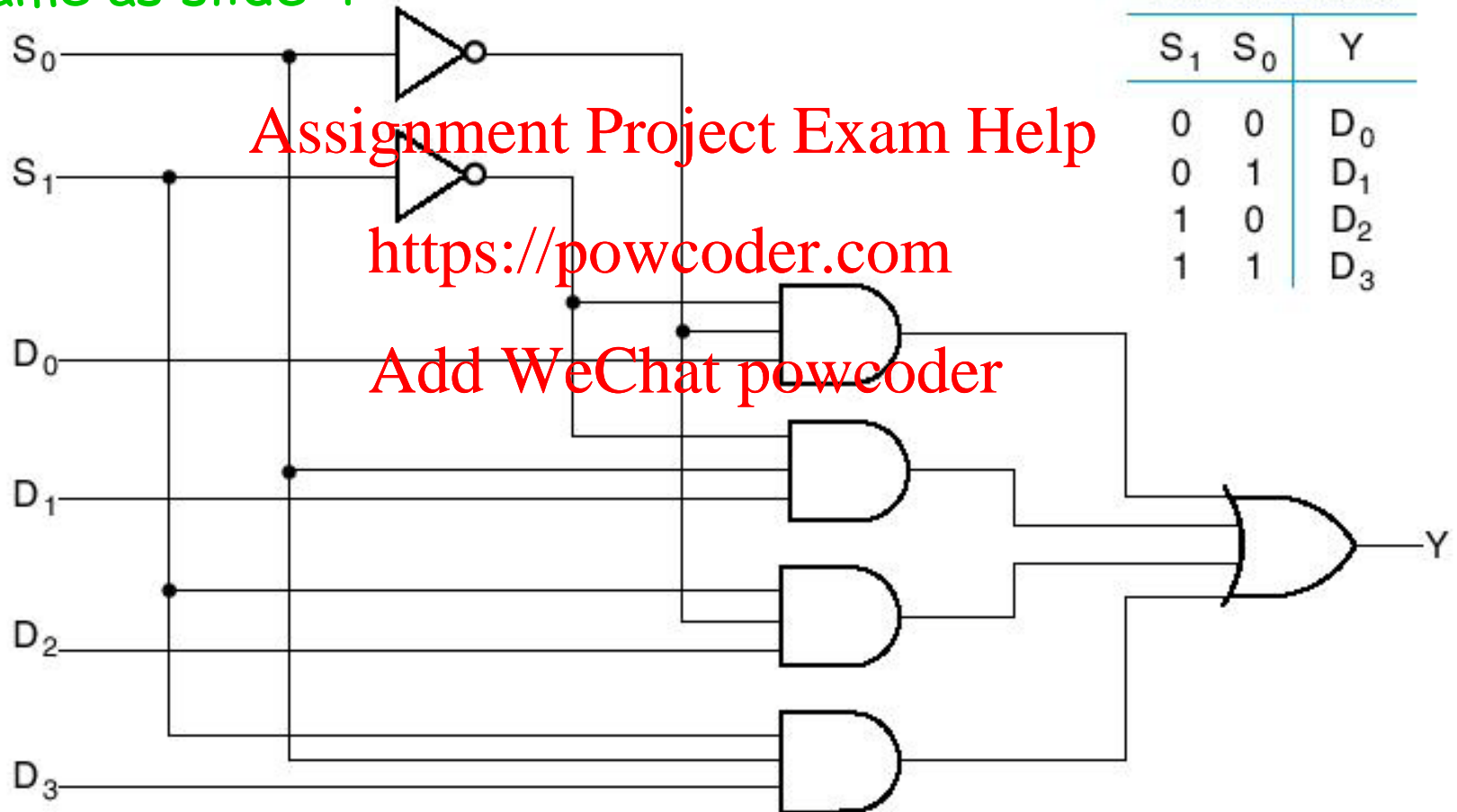

Function table

$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# 4 to 1 Line Multiplexer (Page 1)

## Conditional Dataflow (When-Else)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_we is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_we;

architecture function_table of multiplexer_4_to_1_we is
begin
    Y <= D(0) when S = "00" else
          D(1) when S = "01" else
          D(2) when S = "10" else
          D(3) when S = "11" else
          'X';
end function_table;
```

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# 4 to 1 Line Multiplexer (Page 1)

## Conditional Dataflow (With-Select)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_ws is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_ws;

architecture function_table_ws of multiplexer_4_to_1_ws is
begin
    with S select
        Y <= D(0) when "00",
              D(1) when "01",
              D(2) when "10",
              D(3) when "11",
              'X' when others;
end function_table_ws;
```